

LAB 05

8-Bit Ripple Carry Adder

CECS 225 – DIGITAL LOGIC AND ASSEMBLY PROGRAMMING


Professor: Xiaolong Wu

Student: Thanh Nguyen _ ID: 026843815

1. Introduction:

- *Definition:* 8-bit Ripple Carry Adder is a logic circuit used for adding the 8-bit numbers in digital operations. It is the center of most digital circuits that perform addition or subtraction. It adds together two 8-bit binary digits, plus a carry-in digit to produce a sum and a carry-out digit.
- *Structure:*
 - It has 8 Fully Adders (numbered 0 through 7) tied together.
 - It requires 3 inputs and produces 2 outputs.
 - Three inputs are two 8-bit hexadecimal digits A_8 and B_8, and a 1-bit binary digit called Cin_1.
 - The outputs are the sum of two 8-bit hexadecimal digits, which is an 8-bit output S_8 and a 1-bit digit carry-out is Cout_1
- *Diagram:*

Ripple Carry Adder Diagram

 

2. Function Table with 8 test cases

Inputs				Outputs	
Test Cases	Cin	A_8	B_8	Cout	S_8
0	0	12	34	0	46
1	0	55	AA	0	FF
2	0	72	27	0	99
3	0	80	08	0	88
4	1	12	34	0	47
5	1	55	AA	1	0
6	1	72	27	0	9A
7	1	80	08	0	89

3. Verilog Codes

- *Design Code*

```

module HalfAdder(A, B, Cout, S);
    input A, B;
    output Cout, S;

    assign Cout = A & B;
    assign S = A ^ B;

endmodule

module FullAdder(Cin, FA_A, FA_B, FA_S, FA_Cout);
    input FA_A, FA_B, Cin;
    output FA_S, FA_Cout;

    wire ha0_S, ha0_C, ha1_C;

    HalfAdder ha0 (    .A    (FA_A) ,
                      .B    (FA_B) ,
                      .Cout (ha0_C),
                      .S    (ha0_S)
                    );

    HalfAdder ha1 (    .A    (Cin) ,
                      .B    (ha0_S),
                      .Cout (ha1_C),
                      .S    (FA_S)
                    );

    // This is the carry out for the Full Adder
    assign FA_Cout = ha0_C | ha1_C;

endmodule

module RCA8(A_8, B_8, Cin_1, Cout_1, S_8);

    input      Cin_1;
    input  [7:0] A_8, B_8;

    output [7:0] S_8;
    output      Cout_1;

    wire c0, c1, c2, c3, c4, c5, c6;
    FullAdder fa0(.Cin    (Cin_1),
                  .FA_A    (A_8[0]),
                  .FA_B    (B_8[0]),
                  .FA_S    (S_8[0]),
                  .FA_Cout (c0)
                );

    FullAdder fa1(.Cin    (c0),
                  .FA_A    (A_8[1]),
                  .FA_B    (B_8[1]),
                  .FA_S    (S_8[1]),
                  .FA_Cout (c1)
                );

    FullAdder fa2(.Cin    (c1),

```

```

        .FA_A    (A_8[2]),
        .FA_B    (B_8[2]),
        .FA_S    (S_8[2]),
        .FA_Cout(c2)
    );

    FullAdder fa3(.Cin    (c2),
        .FA_A    (A_8[3]),
        .FA_B    (B_8[3]),
        .FA_S    (S_8[3]),
        .FA_Cout(c3)
    );

    FullAdder fa4(.Cin    (c3),
        .FA_A    (A_8[4]),
        .FA_B    (B_8[4]),
        .FA_S    (S_8[4]),
        .FA_Cout(c4)
    );

    FullAdder fa5(.Cin    (c4),
        .FA_A    (A_8[5]),
        .FA_B    (B_8[5]),
        .FA_S    (S_8[5]),
        .FA_Cout(c5)
    );

    FullAdder fa6(.Cin    (c5),
        .FA_A    (A_8[6]),
        .FA_B    (B_8[6]),
        .FA_S    (S_8[6]),
        .FA_Cout(c6)
    );

    FullAdder fa7(.Cin    (c6),
        .FA_A    (A_8[7]),
        .FA_B    (B_8[7]),
        .FA_S    (S_8[7]),
        .FA_Cout(Cout_1)
    );

endmodule

```

- *Testbench*

```

`timescale 1ns/1ps

module testbench();
    reg      Cin_11;
    reg [7:0] A_81, B_81;

    wire [7:0] S_81;
    wire      Cout_11;

    RCA8 rca(A_81, B_81, Cin_11, Cout_11, S_81);

```

```

initial
begin
    //Dump waves
    $dumpfile("dump.vcd");
    $dumpvars(1, testbench);

    // Cin_1 = 0, A_8 = 12, B_8 = 34
    $display("Test Case 0");
    Cin_11 = 1'b0; A_81 = 8'h12; B_81 = 8'h34;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 0, A_8 = 55, B_8 = AA
    $display("Test Case 1");
    Cin_11 = 1'b0; A_81 = 8'h55; B_81 = 8'hAA;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 0, A_8 = 72, B_8 = 27
    $display("Test Case 2");
    Cin_11 = 1'b0; A_81 = 8'h72; B_81 = 8'h27;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 0, A_8 = 80, B_8 = 8
    $display("Test Case 3");
    Cin_11 = 1'b0; A_81 = 8'h80; B_81 = 8'h8;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 1, A_8 = 12, B_8 = 34
    $display("Test Case 4");
    Cin_11 = 1'b1; A_81 = 8'h12; B_81 = 8'h34;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 1, A_8 = 55, B_8 = AA
    $display("Test Case 5");
    Cin_11 = 1'b1; A_81 = 8'h55; B_81 = 8'hAA;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 1, A_8 = 72, B_8 = 27
    $display("Test Case 6");
    Cin_11 = 1'b1; A_81 = 8'h72; B_81 = 8'h27;
    $display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
    #2
    $display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);

    // Cin_1 = 1, A_8 = 80, B_8 = 8
    $display("Test Case 7");
    Cin_11 = 1'b1; A_81 = 8'h80; B_81 = 8'h8;

```

```

$display("Cin_1 = %b", Cin_11, "      A_8 = %2h", A_81, "      B_8 = %2h", B_81);
#2
$display("Cout_1 = %b", Cout_11, "      S_8 = %2h", S_81);
end
endmodule

```

4. Simulator Waveform

- Inputs and Outputs:

Test Case 0			
Cin_1 = 0	A_8 = 12	B_8 = 34	
Cout_1 = 0	S_8 = 46		
Test Case 1			
Cin_1 = 0	A_8 = 55	B_8 = aa	
Cout_1 = 0	S_8 = ff		
Test Case 2			
Cin_1 = 0	A_8 = 72	B_8 = 27	
Cout_1 = 0	S_8 = 99		
Test Case 3			
Cin_1 = 0	A_8 = 80	B_8 = 08	
Cout_1 = 0	S_8 = 88		
Test Case 4			
Cin_1 = 1	A_8 = 12	B_8 = 34	
Cout_1 = 0	S_8 = 47		
Test Case 5			
Cin_1 = 1	A_8 = 55	B_8 = aa	
Cout_1 = 1	S_8 = 00		
Test Case 6			
Cin_1 = 1	A_8 = 72	B_8 = 27	
Cout_1 = 0	S_8 = 9a		
Test Case 7			
Cin_1 = 1	A_8 = 80	B_8 = 08	
Cout_1 = 0	S_8 = 89		

- Waveform:

