

LAB 04

FULL ADDER

CECS 225 – DIGITAL LOGIC AND ASSEMBLY PROGRAMMING


Professor: Xiaolong Wu

Student: Thanh Nguyen _ ID: 026843815


1. Introduction:

- *Definition:* Full Adder is the center of most digital circuits that perform addition or subtraction. It adds together two binary digits, plus a carry-in digit to produce a sum and a carry-out digit.
- *Structure:*
 - It requires 3 inputs and produces 2 outputs. Three outputs consist 2 binary digits A and B, and a carry-in digit called Cin. The outputs are the sum of 2 binary digits and carry-in known as Cout, and a carry-out digit output.

Half Adder

 

FullAdder

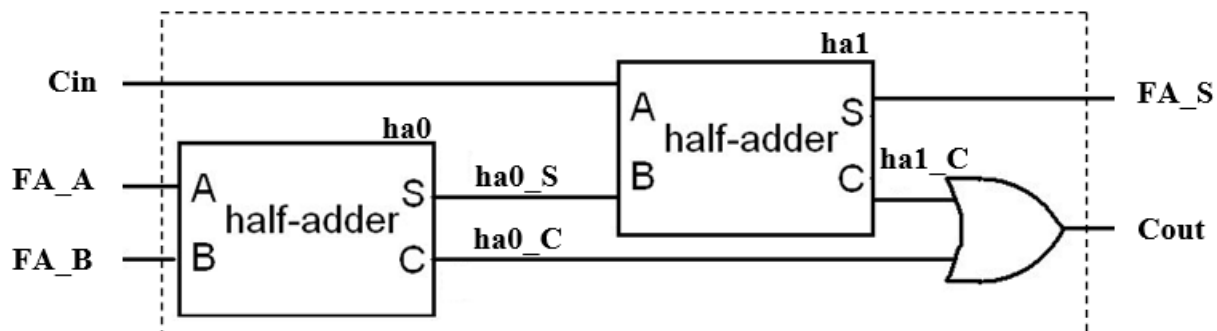

- It is implemented from 2 Half Adders and one OR logic gate. With this logic circuit, 2 bits can be added together, taking a carry from the next lower order of magnitude, and sending a carry to the next higher order of magnitude. As we see in the circuit above, the inputs of Half Adder 1 are a carry-in **Cin** is input **A** and a carry-out from Half Adder 0 **ha0_S** is input **B**. For the outputs, **FA_S** is the final carry-out digit which is **S** and **ha1_C** is the final sum **C**. Then we got:

HalfAdder ha1(.A(Cin), .B(ha0_S), .Cout(ha1_C), .S(FA_S))

- *Truth table:*

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

2. Verilog Codes

- *Design Code*

```

1 // Project 04: Full Adder
2 // Name : Thanh Nguyen - ID: 026843815
3
4 module HalfAdder(A, B, Cout, S);
5     input A, B;
6     output Cout, S;
7
8     assign Cout = A & B;
9     assign S = A ^ B;
10
11 endmodule
12
13 module FullAdder(Cin, FA_A, FA_B, FA_S, FA_Cout);
14     input FA_A, FA_B, Cin;
15     output FA_S, FA_Cout;
16
17     wire ha0_S, ha0_C, ha1_C;
18
19     HalfAdder ha0 ( .A (FA_A) ,
20                    .B (FA_B) ,
21                    .Cout(ha0_C),
22                    .S (ha0_S)
23                    );
24
25     HalfAdder ha1 ( .A (Cin) ,
26                    .B (ha0_S),
27                    .Cout(ha1_C),
28                    .S (FA_S)
29                    );
30
31     // This is the carry out for the Full Adder
32     assign FA_Cout = ha0_C | ha1_C;
33
34 endmodule

```

- *Testbench*

```

1 // Project 04: Full Adder
2 // Name : Thanh Nguyen - ID: 026843815
3
4 `timescale 1ns/1ps
5
6 module testbench();
7     reg FA_A1, FA_B1, Cin1;
8     wire FA_S1, FA_Cout1;
9
10    FullAdder FA1(Cin1, FA_A1, FA_B1, FA_S1, FA_Cout1);
11
12    initial
13    begin
14        //Dump waves
15        $dumpfile("dump.vcd");
16        $dumpvars(1, testbench);
17
18        // Cin = 0, FA_A = 0, FA_B = 0
19        $display("Test Case 0");
20        Cin1 = 1'b0; FA_A1 = 1'b0; FA_B1 = 1'b0;
21        $display("Cin = %b", Cin1, " FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
22        #1
23        $display("FA_Cout = %b", FA_Cout1, " FA_S = %b",
FA_S1);
24
25        // Cin = 0, FA_A = 0, FA_B = 1
26        $display("Test Case 1");
27        Cin1 = 1'b0; FA_A1 = 1'b0; FA_B1 = 1'b1;
28        $display("Cin = %b", Cin1, " FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
29        #1
30        $display("FA_Cout = %b", FA_Cout1, " FA_S = %b",
FA_S1);
31
32        // Cin = 0, FA_A = 1, FA_B = 0
33        $display("Test Case 2");
34        Cin1 = 1'b0; FA_A1 = 1'b1; FA_B1 = 1'b0;
35        $display("Cin = %b", Cin1, " FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
36        #1
37        $display("FA_Cout = %b", FA_Cout1, " FA_S = %b",
FA_S1);

```

SV/Verilog Testbench

```

38
39     // Cin = 0, FA_A = 1, FA_B = 1
40     $display("Test Case 3");
41     Cin1 = 1'b0; FA_A1 = 1'b1; FA_B1 = 1'b1;
42     $display("Cin      = %b", Cin1, "      FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
43     #1
44     $display("FA_Cout = %b", FA_Cout1, "      FA_S = %b",
FA_S1);
45
46     // Cin = 1, FA_A = 0, FA_B = 0
47     $display("Test Case 4");
48     Cin1 = 1'b1; FA_A1 = 1'b0; FA_B1 = 1'b0;
49     $display("Cin      = %b", Cin1, "      FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
50     #1
51     $display("FA_Cout = %b", FA_Cout1, "      FA_S = %b",
FA_S1);
52
53     // Cin = 1, FA_A = 0, FA_B = 1
54     $display("Test Case 5");
55     Cin1 = 1'b1; FA_A1 = 1'b0; FA_B1 = 1'b1;
56     $display("Cin      = %b", Cin1, "      FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
57     #1
58     $display("FA_Cout = %b", FA_Cout1, "      FA_S = %b",
FA_S1);
59
60     // Cin = 1, FA_A = 1, FA_B = 0
61     $display("Test Case 6");
62     Cin1 = 1'b1; FA_A1 = 1'b1; FA_B1 = 1'b0;
63     $display("Cin      = %b", Cin1, "      FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
64     #1
65     $display("FA_Cout = %b", FA_Cout1, "      FA_S = %b",
FA_S1);
66
67     // Cin = 1, FA_A = 1, FA_B = 1
68     $display("Test Case 7");
69     Cin1 = 1'b1; FA_A1 = 1'b1; FA_B1 = 1'b1;
70     $display("Cin      = %b", Cin1, "      FA_A = %b", FA_A1, "
FA_B = %b", FA_B1);
71     #1
72     $display("FA_Cout = %b", FA_Cout1, "      FA_S = %b",
FA_S1);
73     end
74
75 endmodule

```

3. Simulator Waveform

- *Half Adder:*


- Inputs and Outputs:

```

Test Case 0
A   = 0    B = 0
Cout = 0    F = 0
Test Case 1
A   = 0    B = 1
Cout = 0    F = 1
Test Case 2
A   = 1    B = 0
Cout = 0    F = 1
Test Case 3
A   = 1    B = 1
Cout = 1    F = 0

```

○ Waveform:

 

- **Full Adder:**

○ Inputs and Outputs:

```

Test Case 0
Cin   = 0    FA_A = 0    FA_B = 0
FA_Cout = 0    FA_S = 0
Test Case 1
Cin   = 0    FA_A = 0    FA_B = 1
FA_Cout = 0    FA_S = 1
Test Case 2
Cin   = 0    FA_A = 1    FA_B = 0
FA_Cout = 0    FA_S = 1
Test Case 3
Cin   = 0    FA_A = 1    FA_B = 1
FA_Cout = 1    FA_S = 0
Test Case 4
Cin   = 1    FA_A = 0    FA_B = 0
FA_Cout = 0    FA_S = 1
Test Case 5
Cin   = 1    FA_A = 0    FA_B = 1
FA_Cout = 1    FA_S = 0
Test Case 6
Cin   = 1    FA_A = 1    FA_B = 0
FA_Cout = 1    FA_S = 0
Test Case 7
Cin   = 1    FA_A = 1    FA_B = 1
FA_Cout = 1    FA_S = 1

```

○ Waveform:

